# University of Colorado Boulder ECEE Department

ECEN 2350 - Digital Logic - Fall 2023

Location: Engineering Center, ECCR 1B40, MWF 1:25PM - 2:15PM

**Instructor:** Dr. Mona ElHelbawy

Lab #2

Lab Title: Design a 4-bit RCA using Vivado SystemVerilog

Date of Experiment: September 25th, 2023

Names: Connor Sorrell

# Part 1

#### Description:

- In this lab, we will experiment and work with three different modules. These will be a 2-bit half adder, a 3-bit full adder, and a ripple carry adder (RCA).

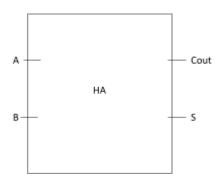


Figure 1.1.0: Black Box Diagram showing the 2 inputs (A,B) and the output S, and carryout, C. This circuit adds two bits.

#### Truth Table:

- This table shows the boolean logic and function values for each combination of inputs. As seen, the half adder adds the two inputs. If the sum is 1, the output, S will be 1. If the sum is 0, the output, S is 0. If the sum is 2, the output, S, will be 1, and the carry out will be 1.

index	А	В	S	Cout
0	0	0	0	0
1	0	1	1	0
2	1	0	1	0
3	1	1	1	1

Figure 1.1.1: Truth table representing the boolean logic present in the half adder. (This will add two binary bits)

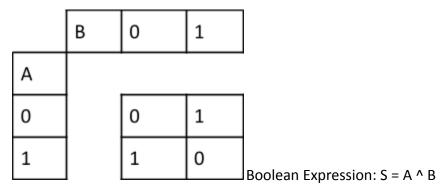


Figure 1.1.2: K-map for S

# K-map for C:

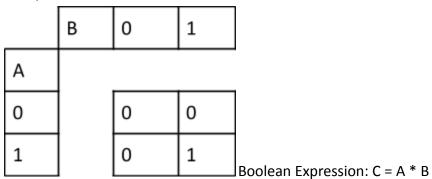


Figure 1.1.3: K-map for C

 


Figure 1.1.4: Schematic of the Half Adder circuit. Showcases two inputs, an XOR gate leading to an output, and an AND gate leading to the carryout output.



Figure 1.1.5: Timing diagram for the Half Adder. Showcases all possible inputs and their outputs.

```
module HA(
   input A,
   input B,
   output S,
   output C
  );
   assign S = A^B;
   assign C = AsB;
endmodule
```

Figure 1.1.6: Source code for the half adder circuit. Shows the 2 inputs, 2 outputs, and the boolean logic.

```
module HAsim();
   logic A, B, S, C;
   HA HAinst(.*);
   //list test cases
   initial
       begin
       A = 0; B = 0;
       #10
       if (S!==0||C!==0) $display ("Error");
        #10
       if (S!==1||C!==0) $display ("Error");
       A=1; B=0;
       if(S!==1||C!==0)$display("Error");
       A=1; B=1;
       if(S!==0||C!==1)$display("Error");
       $display("Finished");
endmodule
```

Figure 1.1.7: Simulation code for the half adder circuit. Shows each test case.

# Part 2

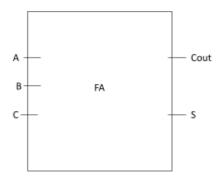



Figure 1.2.0: Black Box Diagram showing the 3 inputs (A,B,C) and output S, and carryout, C. This circuit will add three binary bits.

# Truth Table:

- This table shows the boolean logic and function values for each combination of inputs. As seen, the full adder adds the three inputs. If the sum is 1, the output, S will be 1. If the sum is 0, the output, S is 0. If the sum is 2, the output, S, will be 1, and the carry out will be 1.

index	А	В	S	Cout
0	0	0	0	0
1	0	1	1	0
2	1	0	1	0
3	1	1	1	1

Figure 1.2.1: Truth table representing the boolean logic present in the full adder. (This will add three binary bits)

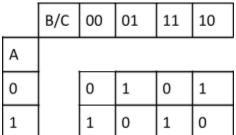

 $\bot$ Boolean Expression: S = A ^ B ^ C

Figure 1.2.2: K-map for S

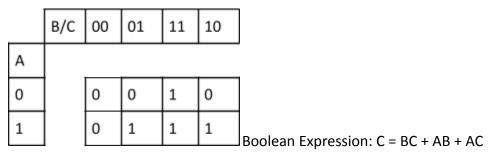


Figure 1.2.3: K-map for C

 


Figure 1.2.4: Schematic of the Full Adder circuit.



Figure 1.2.5: Timing diagram for the Full Adder. Showcases all possible inputs and their outputs.

```
module FA(
   input A,
   input B,
   input C,
   output S,
   output CO
   );
   assign S = (A ^ B ^ C);
   assign CO = (A&B) | (A&C) | (B&C);
endmodule
```

Figure 1.2.6: Source code of the Full Adder. Showcases the three inputs, two outputs, and the boolean logic behind the circuit.

```
module FAsim();
   logic A, B, C, S, CO;
   FA FAinst(.*);
    //list test cases
   initial
        A = 0; B = 0; C = 0;
        if(S!==0||C0!==0)$display("Error");
        A = 0; B = 0; C = 1;
        #10
        if (S!==1||C0!==0) $display ("Error");
        A = 0; B = 1; C = 0;
        #10
        if (S!==1||C0!==0) $display ("Error");
        A = 0; B = 1; C = 1;
        #10
        if(S!==0||C0!==1)$display("Error");
        A = 1; B = 0; C = 0;
        if (S!==1||C0!==0) $display ("Error");
        A = 1; B = 0; C = 1;
        if (S!==0||C0!==1) $display ("Error");
        A = 1; B = 1; C = 0;
        if (S!==0||C0!==1) $display ("Error");
        A = 1; B = 1; C = 1;
        if (S!==1||C0!==1) $display ("Error");
        $display("Finished");
```

Figure 1.2.7: Simulation code for the Full Adder. Showcases each test case.

# Part 3

# **Description:**

- In this lab, we will experiment and work with three different modules. These will be a 2-bit half adder, a 3-bit full adder, and a ripple carry adder (RCA).

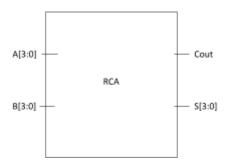


Figure 1.3.0: Black Box Diagram showing the 2 inputs (A[3:0],B[3:0]) and the output S[3:0], and carryout, C

 


Figure 1.3.1: RCA structural model diagram

 


Figure 1.3.2: Schematic diagram of the RCA circuit. Showcases the structure of the circuit, the inputs and outputs.

 


Figure 1.3.3: Timing diagram of the RCA circuit. Showcases the possible inputs and their respective results.

```
module RCA1(
   input [3:0]A,
   input [3:0]B,
   output [3:0]S,
   output CO
);
   logic t1,t2,t3;

HA HAO (.A(A[0]), .B(B[0]), .S(S[0]), .C(t1));
   FA FA1 (.A(A[1]), .B(B[1]), .C(t1), .S(S[1]), .CO(t2));
   FA FA2 (.A(A[2]), .B(B[2]), .C(t2), .S(S[2]), .CO(t3));
   FA FA3 (.A(A[3]), .B(B[3]), .C(t3), .S(S[3]), .CO(CO));
endmodule
```

Figure 1.3.4: Source code of the ripple carry adder. Showcases the inputs, and logic behind the circuit.

```
module RCAlsim(
   );
    logic[3:0] A, B, S;
    logic CO;
    RCAl RCAl inst(.*);
    initial
    begin
   //test 1
   A = 5;
    B = 3;
    #10
    if (S !== 8 && CO !== 0) $display ("Error A%h B%h", A, B);
    //test 2
   A = 8;
    B = 9;
    #10
    if ( S !== 1 && CO !== 1) $display ("Error A%h B%h", A, B);
    $display("Finished");
    end
endmodule
```

Figure 1.3.5: Simulation code of the RCA circuit. Showcases the two test cases.